

stomp-chargepump

Project Report

1. Readme

Chargepump/stomp board.


- prevents reverse polarity
- 3pdt + led
- -9v optional out
- 18v optional out
- Both ICL7660 and LT1054

This has been tested but not thoroughly. This layout is based on several vero layout on Tagboardeffects.blogspot.com


2nd revision of this to use 4pin connectors for wiring simplicity

All registered trademarks are owned by their respective owners.


2. Schematic

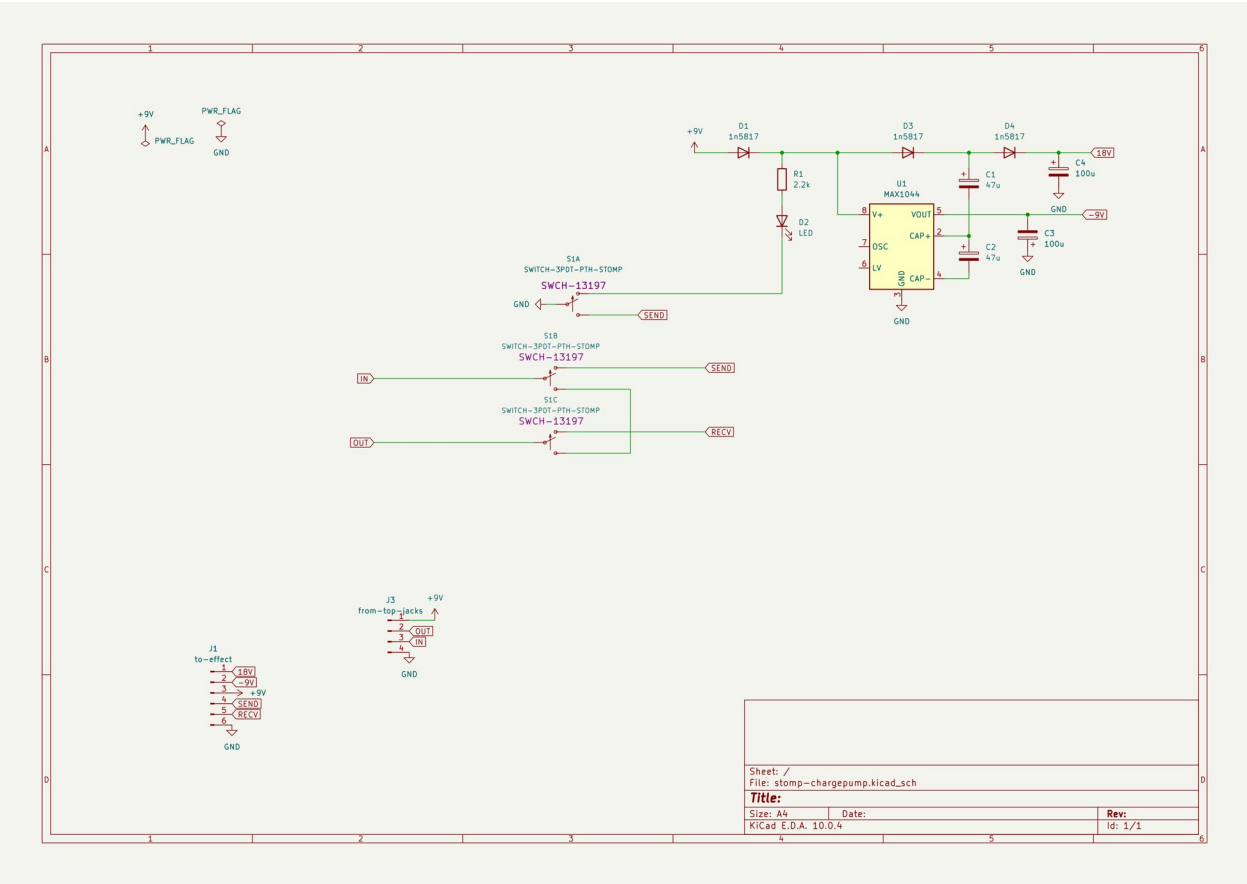

3. PCB F.Cu + Silkscreen

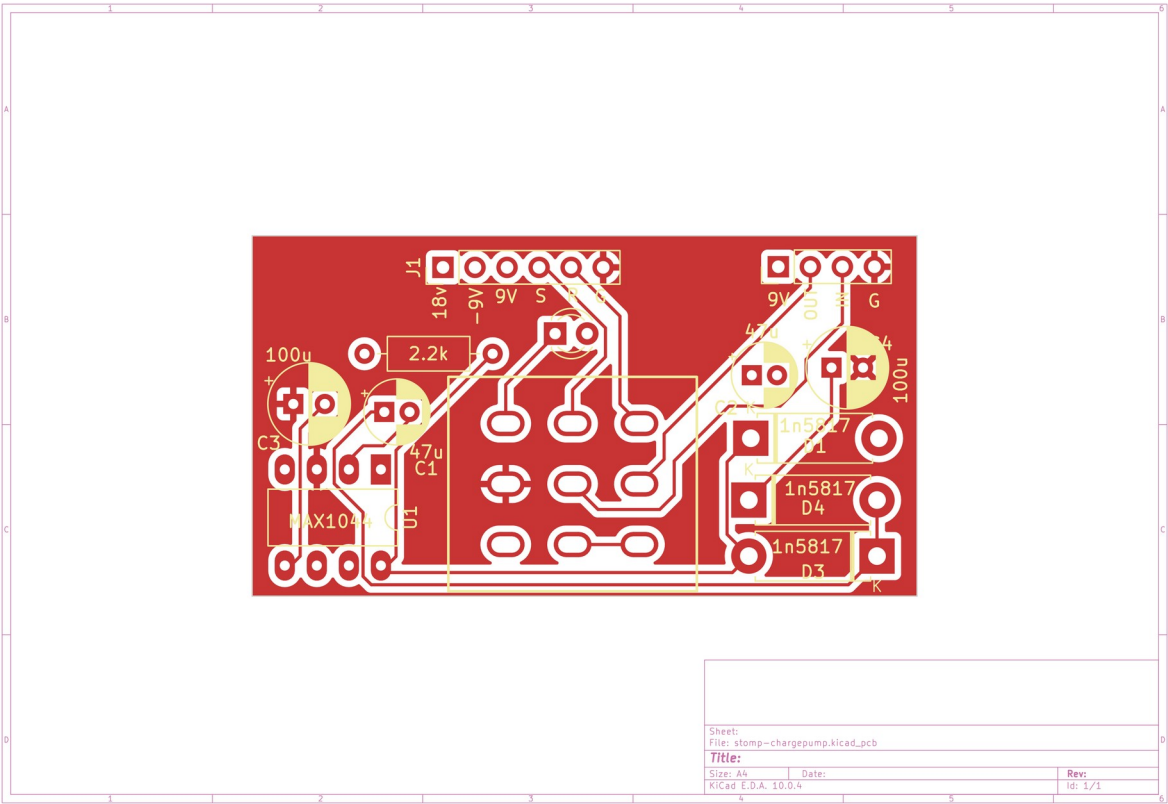

4. PCB B.CU + Silkscreen

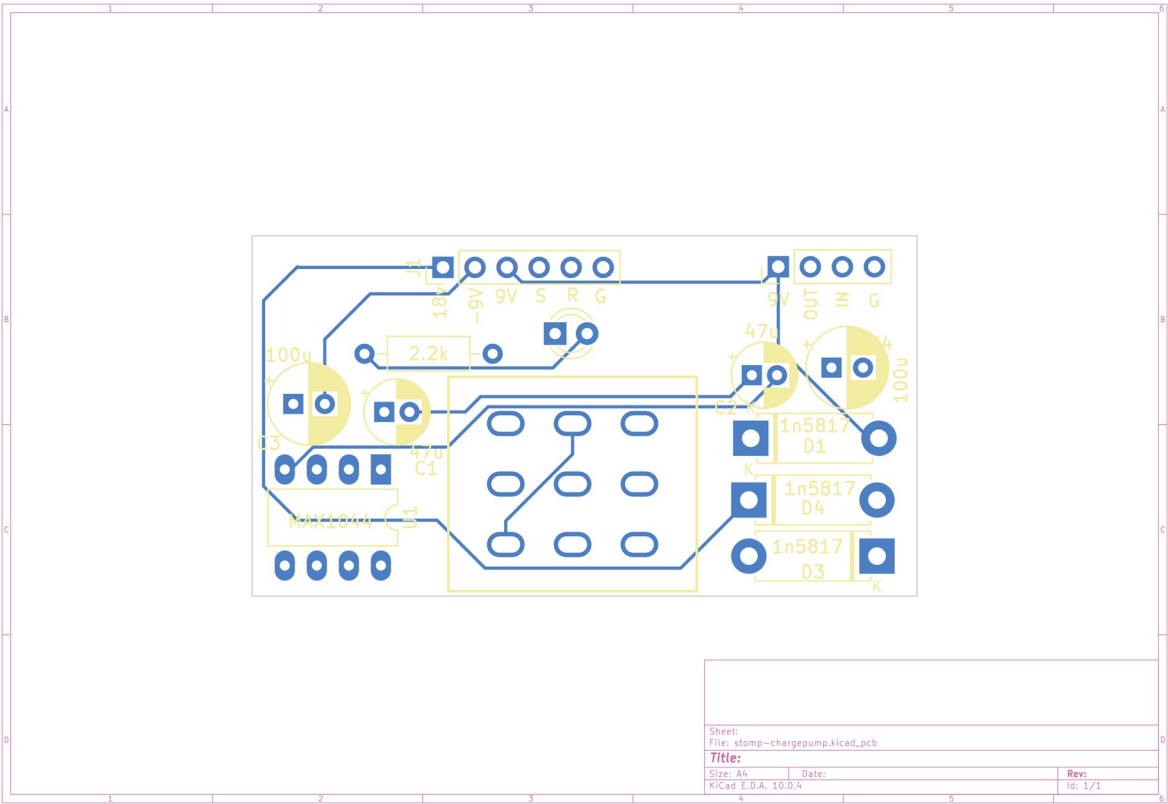

5. Bill of Materials

Reference	Value	Footprint	Qty	DNP
C1,C2	47u	Capacitor_THT: CP_Radial_D5.0mm_P2.00mm	2	
C3,C4	100u	Capacitor_THT: CP_Radial_D6.3mm_P2.50mm	2	
D1,D3,D4	1n5817	Diode_THT:D_5W_P10.16mm_Horizontal	3	
D2	LED	LED_THT:LED_D3.0mm	1	
J1	to-effect	Connector_PinHeader_2.54mm:PinHeader_1x06_P2.54mm_Vertical	1	
J3	from-top-jacks	Connector_PinHeader_2.54mm:PinHeader_1x04_P2.54mm_Vertical	1	
R1	2.2k	Resistor_THT: R_Axial_DIN0207_L6.3mm_D2.5mm_P10.16mm_Horizontal	1	
S1	SWITCH-3PDT-PTH-STOMP	Switches:STOMP_SWITCH_3PDT	1	
U1	MAX1044	Package_DIP: DIP-8_W7.62mm_LongPads	1	

Total line items: 9