


Distortion-02-LQ

Project Report


1. Readme

Distortion pedal based on the Lizard Queen

Schematic

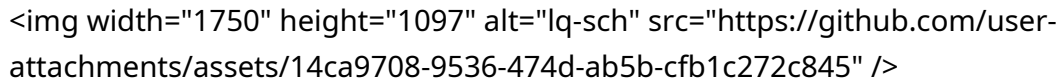
The schematic diagram shows the internal circuitry of the distortion pedal, including the Lizard Queen op-amp, various resistors, capacitors, and the input/output jacks.

pcb layout

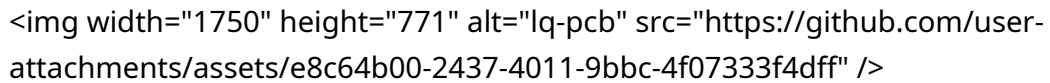
The PCB layout shows the physical arrangement of components on the printed circuit board, including the Lizard Queen op-amp, resistors, capacitors, and the input/output jacks.

All trademarks belong to their respective owners.


2. Schematic

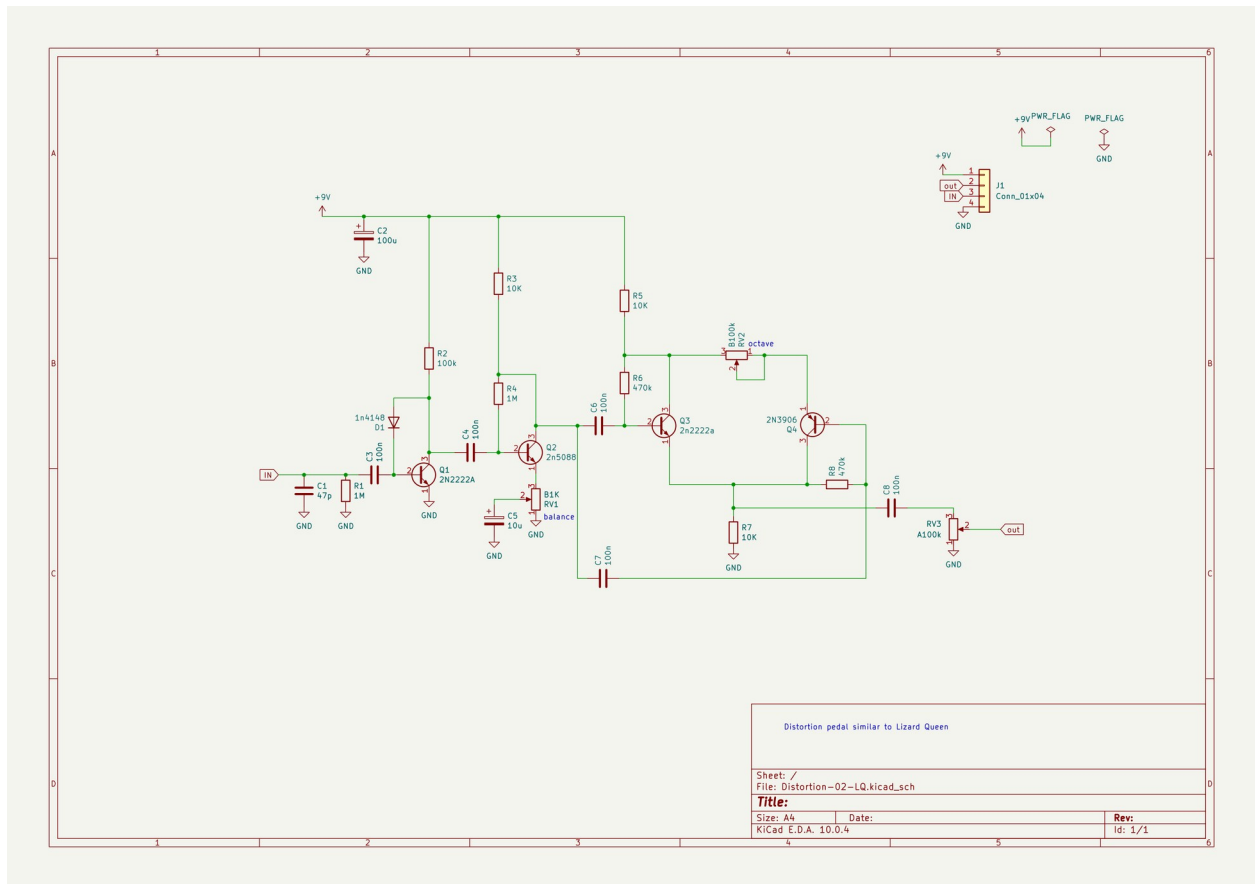

3. PCB F.Cu + Silkscreen

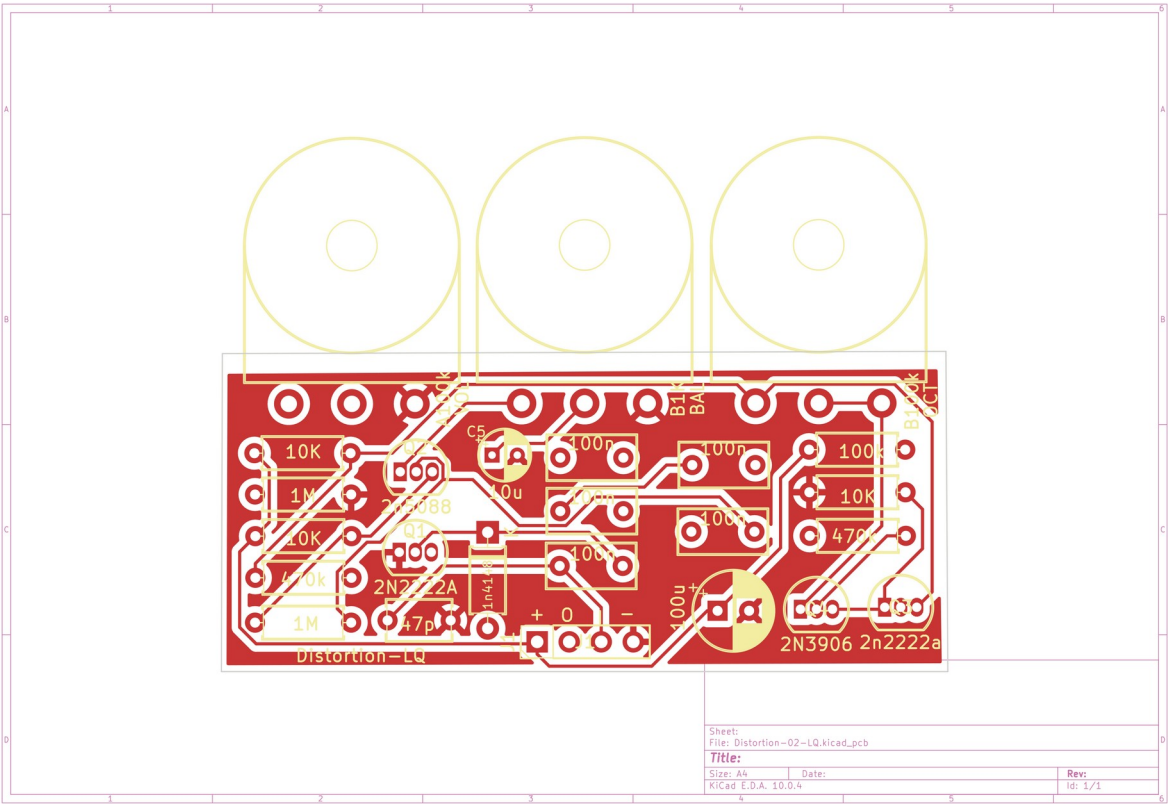

4. PCB B.CU + Silkscreen

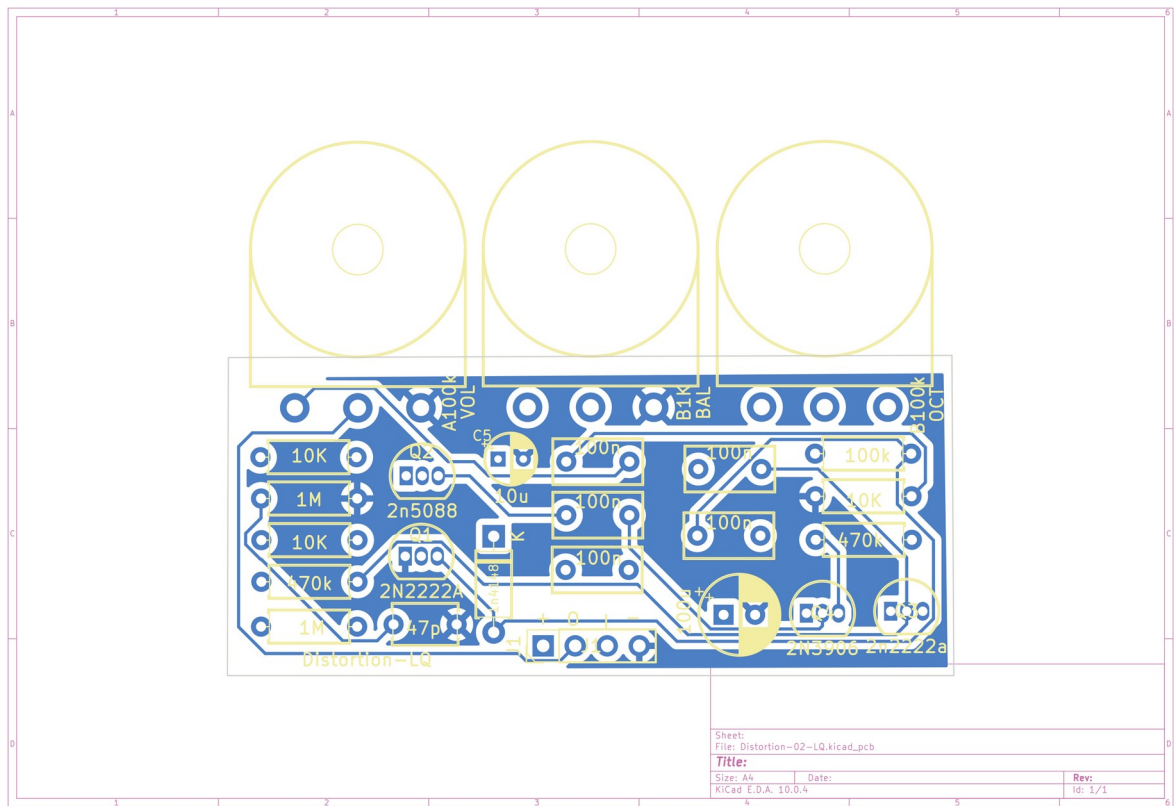

5. Bill of Materials

Reference	Value	Footprint	Qty	DNP
C1	47p	Capacitor_THT: C_Disc_D5.1mm_W3.2mm_P5.00mm	1	
C2	100u	Capacitor_THT: CP_Radial_D6.3mm_P2.50mm	1	
C3,C4,C6-C8	100n	Capacitor_THT: C_Rect_L7.0mm_W3.5mm_P5.00mm	5	
C5	10u	Capacitor_THT: CP_Radial_D4.0mm_P2.00mm	1	
D1	1n4148	Diode_THT:D_A-405_P7.62mm_Horizontal	1	
J1	Conn_01x04	Connector_PinHeader_2.54mm:PinHeader_1x04_P2.54mm_Vertical	1	
Q1	2N2222A	Package_TO_SOT_THT:TO-92_Inline	1	
Q2	2n5088	Package_TO_SOT_THT:TO-92_Inline	1	
Q3	2n2222a	Package_TO_SOT_THT:TO-92_Inline	1	
Q4	2N3906	Package_TO_SOT_THT:TO-92_Inline	1	
R1,R4	1M	Resistor_THT: R_Axial_DIN02	2	

		07_L6.3mm_D 2.5mm_P7.62 mm_Horizont al		
R2	100k	Resistor_THT: R_Axial_DIN02 07_L6.3mm_D 2.5mm_P7.62 mm_Horizont al	1	
R3,R5,R7	10K	Resistor_THT: R_Axial_DIN02 07_L6.3mm_D 2.5mm_P7.62 mm_Horizont al	3	
R6,R8	470k	Resistor_THT: R_Axial_DIN02 07_L6.3mm_D 2.5mm_P7.62 mm_Horizont al	2	
RV1	B1K	Potentiometer _THT:Potentio meter_Omeg_ PC16BU_Verti cal	1	
RV2	B100k	Potentiometer _THT:Potentio meter_Omeg_ PC16BU_Verti cal	1	
RV3	A100k	Potentiometer _THT:Potentio meter_Omeg_ PC16BU_Verti cal	1	

Total line items: 17